

Logic Design Laboratory

Final project announcement
May 21st, 2019

Prof. Jae W. Lee (jaewlee@snu.ac.kr)
Architecture and Code Optimization (ARC) Lab.
Seoul National University

TA: Jeonghun Gong, Yeonhong Park
Myeongseok Seong, Sunmin Jeong


Contents

- **Introduction to simple 8-bit microprocessor**
- **Project Overview**
- **Architecture**
 - Data Path
 - ISA(Instruction Set Architecture)
- **Implementation Guide**
- **Grading Policy**
- **Submission Guide**

Introduction to 8-bit microprocessor

■ What is 8-bit microprocessor?

 - It reads program from memory and operates as it directs.
- Data is also stored on and loaded from memory.
- Basic data size is 8-bit.
 - It reads, processes and writes 8-bit data.
 - It has several 8-bit registers.




MOS Technology 6502 microprocessor (1975)

Introduction to 8-bit microprocessor


- Your microprocessor reads, decodes program and execute it.
 - Program is a sequence of instructions
 - Instruction contains all the information about what should be done by microprocessor

Machine code* (Instruction)

 01000100
01100100
11010000
11010000
11010010
10000100
...



Decode, and Execute!

 

What is done inside

$r0 = r1[0]$
 $r2 = r1[0]$
 $r0 = r0 + r0$
 $r0 = r0 + r0$
 $r0 = r0 + r2$
 $r1[0] = r0$
...

*Not actual MOS 6502 machine code


Project Overview

- Implement a Simple Microprocessor in Verilog and program it in FPGA. Mimic a real computer.
- Implement each component as a module in Verilog. You should make Register, ALU, Control unit, Program Counter, and the other components into separate modules.
- Connect each module in a proper way using bus.
- This is an **individual project**. You **must not** share your code with your partner. Your partnership is officially over!

Project Overview


- 8-bit Microprocessor
 - Instruction size: 8-bit
 - Register & Data size : 8-bit
- # of instructions : 6 (add, sub load, store, jump, nop) + 1 (addi)
- # of registers : 4
- Grading target : Final state of data memory
 - Data memory values (total #: 32) after test sequence of instructions will be compared to the correct answers precalculated by TAs.

Architecture: Data Path

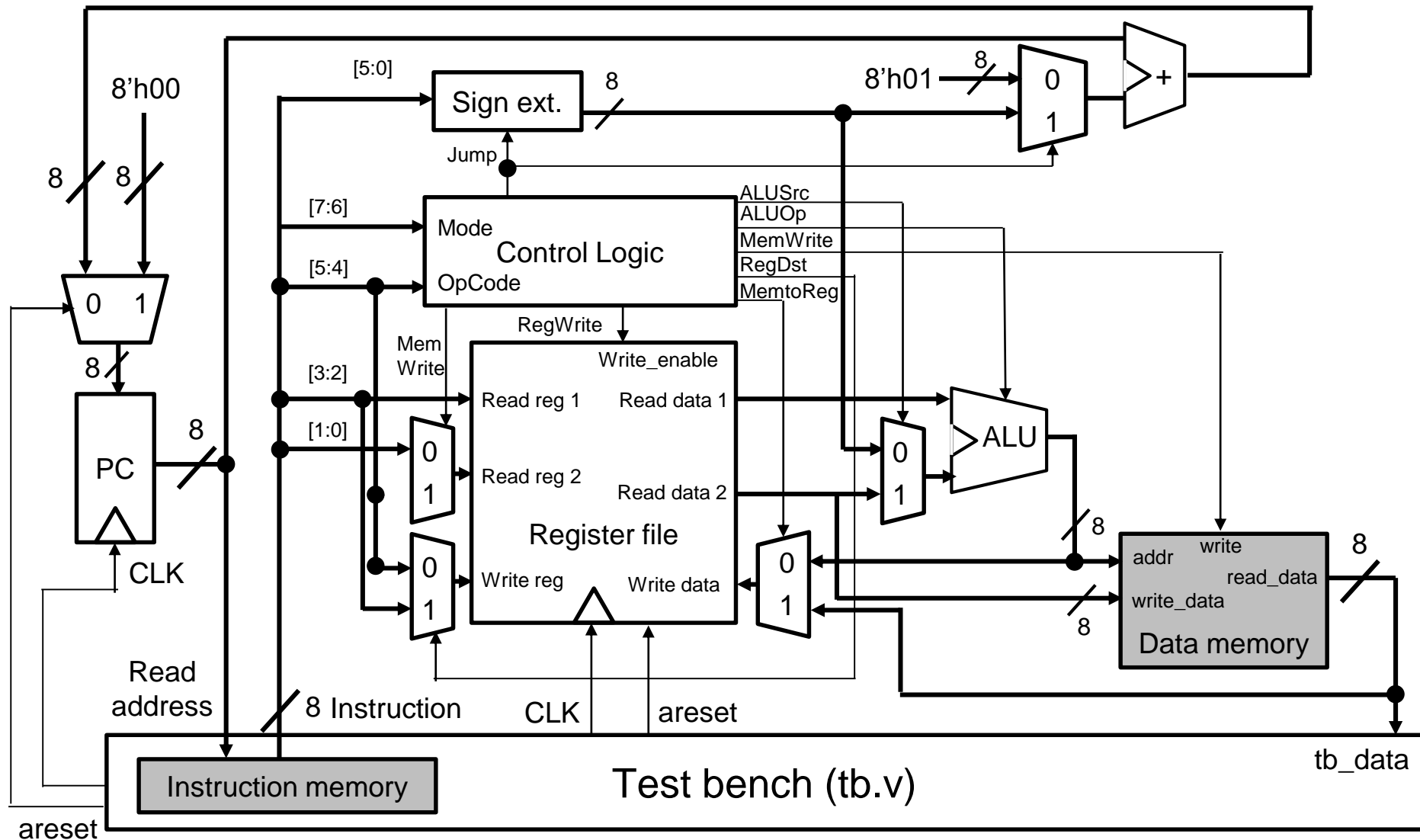


Architecture: PC

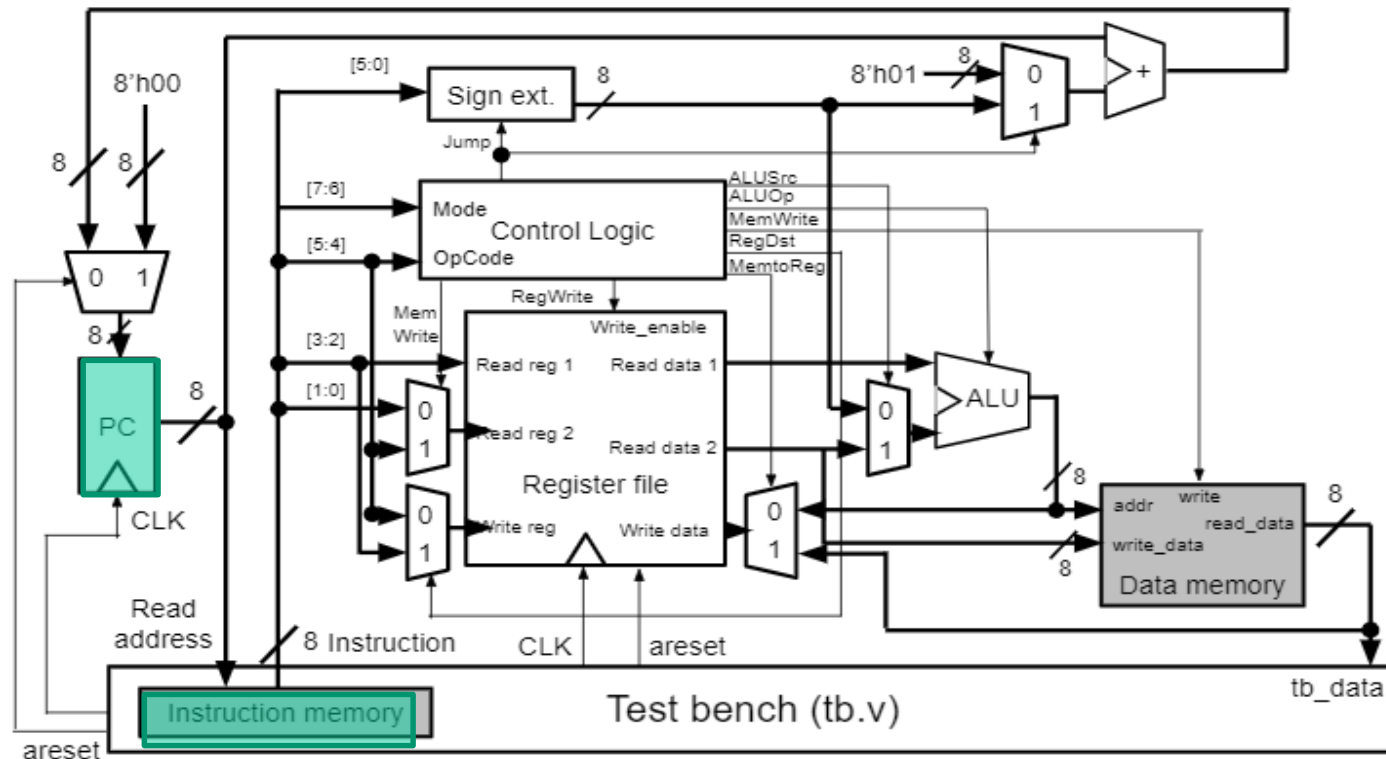- It should have special register “PC (program counter)”
 - PC contains the address of current instruction to fetch from instruction memory, and increment the address by one unless there is a control transfer instruction (‘jump’ in this architecture).



Architecture: Register File

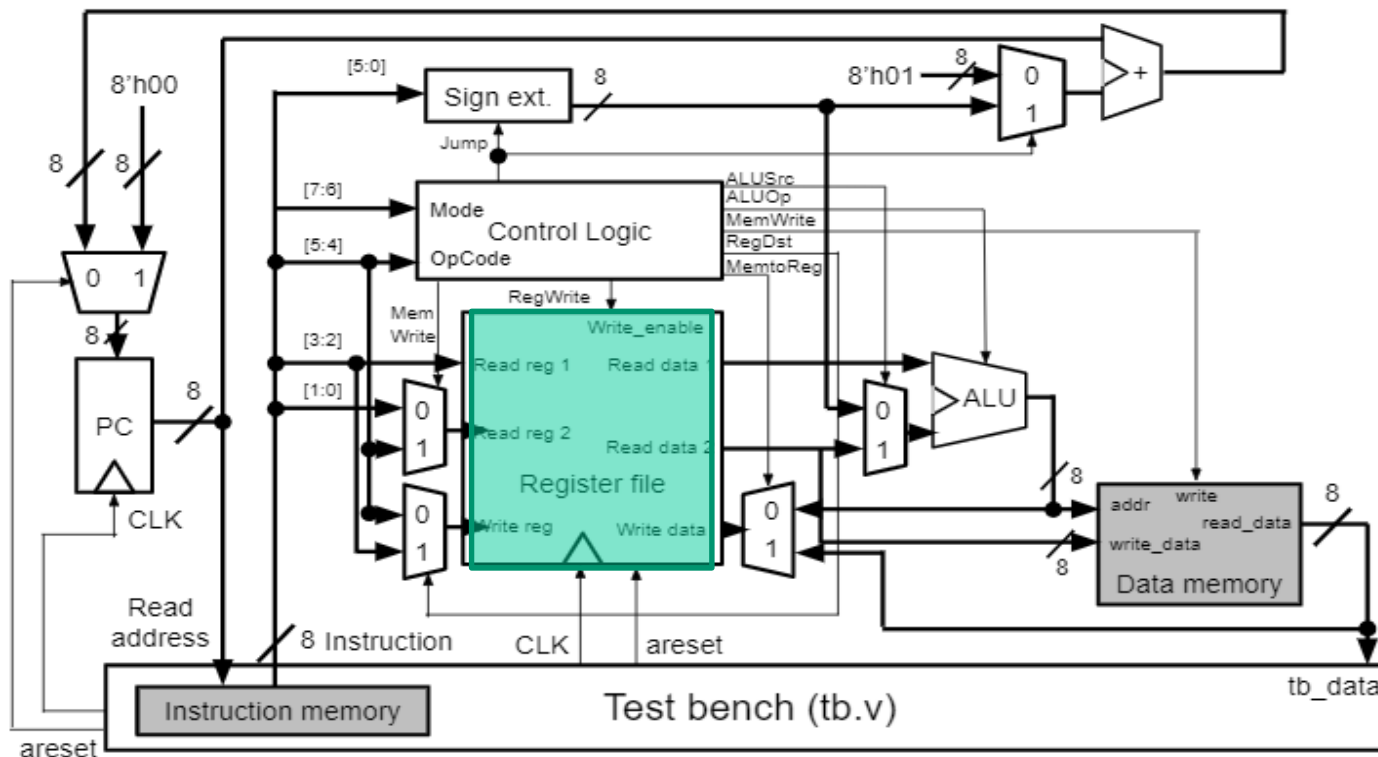
- It has four registers (r0 to r3) in the register file.
 - Register to be read/written is selected by “read reg/write reg” signals. It has two read port and one write port.
 - Register value is updated if write enable is on.



Architecture: Control Logic

■ Control logic

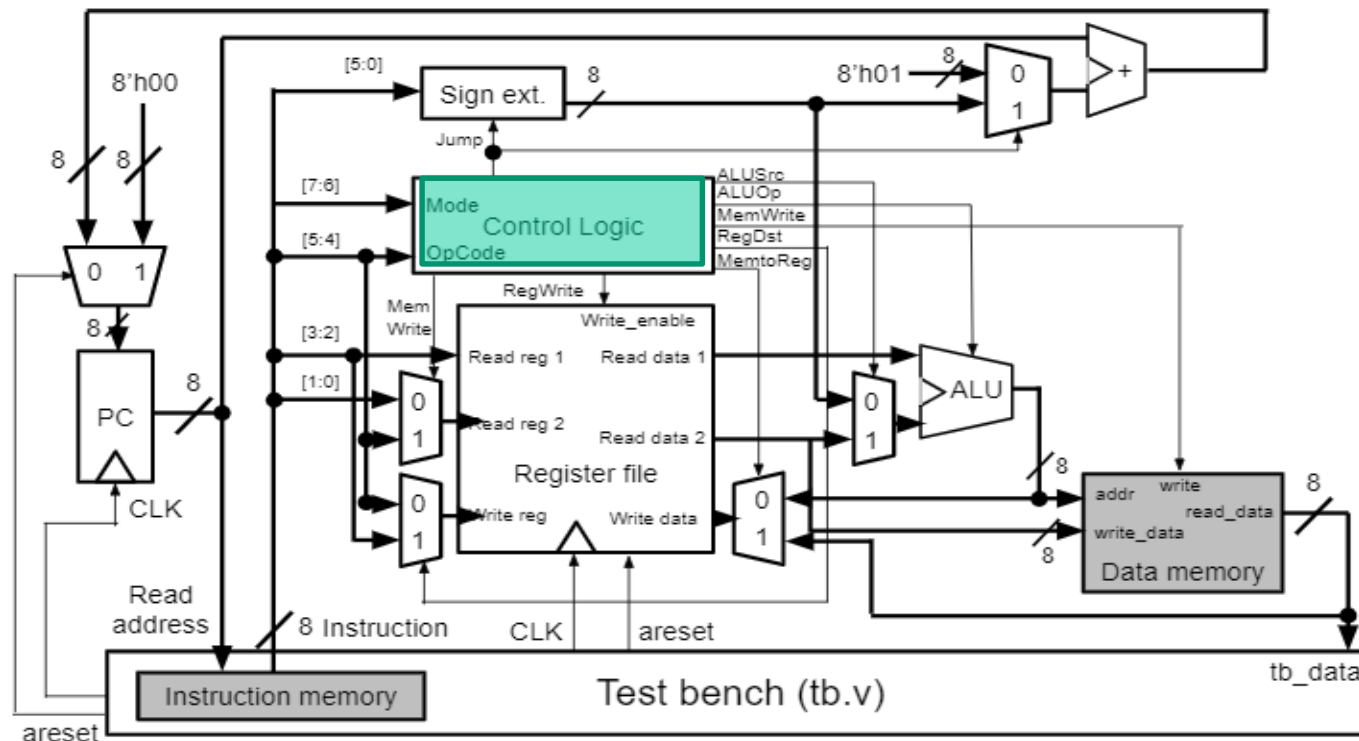
- Control logic decodes instruction and sends out control signals across the microprocessor.



Architecture: Sign Extension Unit

■ Sign extension unit.

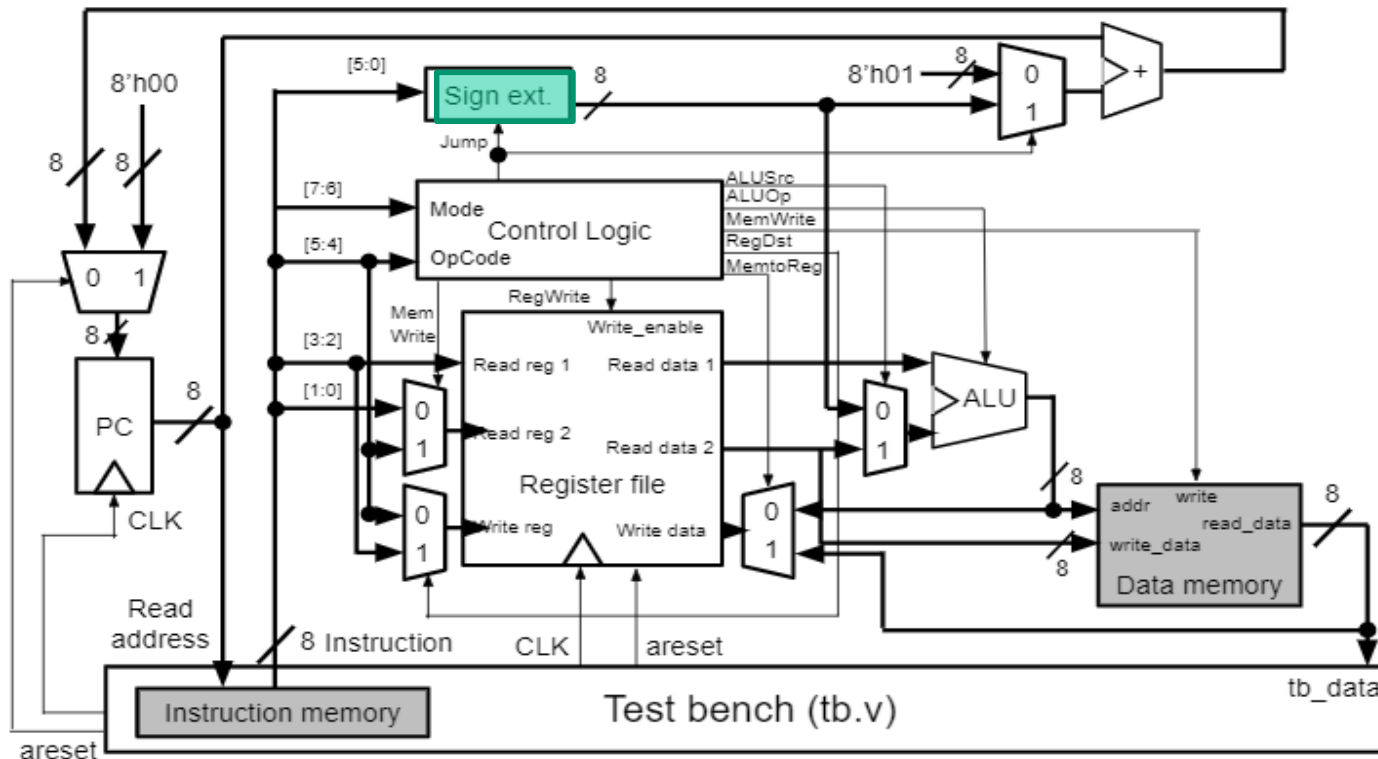
- Used for sign extension of [off] field in load, store and jump instructions.



Architecture: ALU

■ Arithmetic Logic Unit

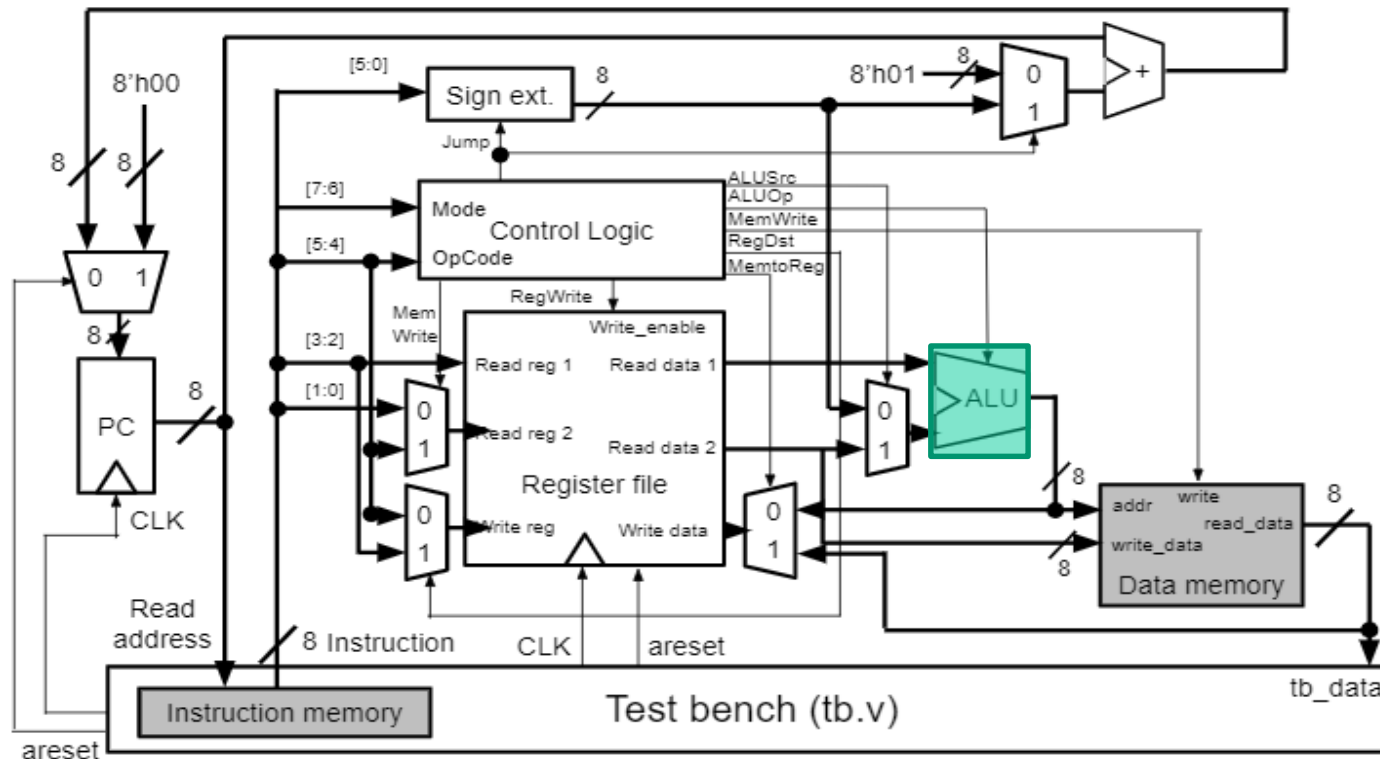
- ALU receives two inputs and execute arithmetic operation based on the control signal.



Architecture: Data Memory

■ Data memory (given)

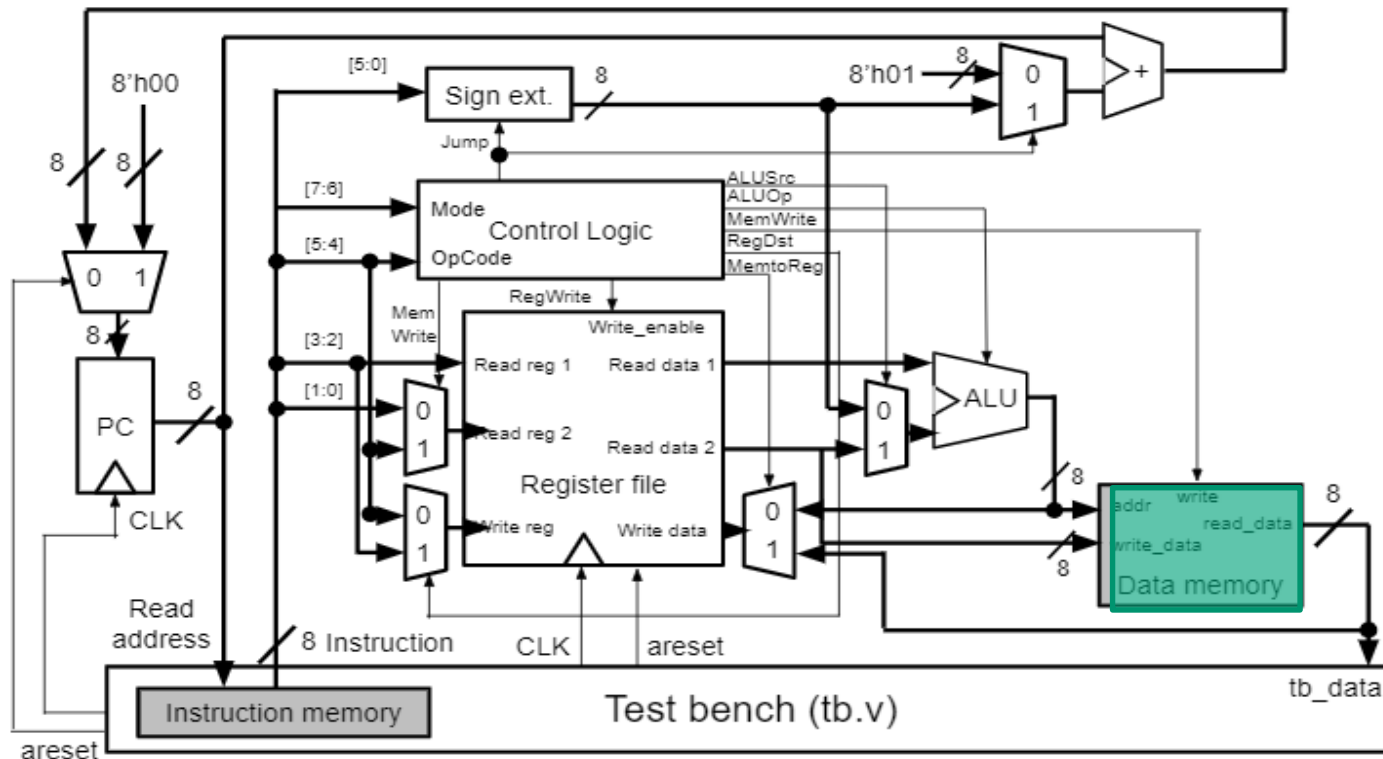- You can write to or read from certain address in data memory.
- Set 'write' bit high when writing. (low when reading)
 - Your data will be updated at rising edge of clk.



Architecture: ISA

■ ISA(Instruction Set Architecture)

- ISA is a set of the instructions that a processor understands. It specifies how each binary code should be interpreted. It is an interface between software and hardware
- In this microprocessor, each instruction is 8-bit and 6 different instructions should be handled.
(Add / Sub / Load/ Store / Jump / NOP)

Architecture: ISA

Type	Opcode	Description	Note
Add	11 01 [rd] [rs]	$\$rd = \$rd + \$rs$	
Sub	11 10 [rd] [rs]	$\$rd = \$rd - \$rs$	
Load	01 [rt] [rs] [off]	$\$rt = \text{mem}[\$rs + \text{off}]$	'off' is sign extended
Store	10 [rs] [rd] [off]	$\text{mem}[\$rd + \text{off}] = \rs	'off' is sign extended
Jump*	00 [off (6 bits)]*	$\$PC = \$PC + \text{off}$	'off' is sign extended
NOP	11 00 XX XX	Do nothing	

Reg. no	Reg. code
r0	00
r1	01
r2	10
r3	11

* Instructions other than Jump should increment PC by 1.


* [...] field is 2 bits except for jump operation.

Implementing Guide

- **Implement your design based on 'cpu.v'**
 - Implement all the components previously explained (except data memory).
 - Make sure not to modify port declaration.
 - Read comments carefully for further instructions.

Implementing Guide: Test by yourself!

 - **Make a project with given tb.v and your cpu.v**
 - Program it on the board.
 - Refer to tb.v:[5-25] for pin mapping.
- **tb.v has three test cases.**
 - Each tactile switch corresponds to certain test case.
 - Seven segment displays will show result.



Bonus stage: Expanded instruction set

■ Addi (Add immediate) instruction

- You will get extra credit (10% of final project credit) for this.
- If your final project score goes over 100%, the surplus will be added to your lab score (not overall course score).

Type	Opcode	Description	Note
Add	11 01 [rd] [rs]	$\$rd = \$rd + \$rs$	
Sub	11 10 [rd] [rs]	$\$rd = \$rd - \$rs$	
Load	01 [rt] [rs] [off]	$\$rt = \text{mem}[\$rs + \text{off}]$	'off' is sign extended
Store	10 [rs] [rd] [off]	$\text{mem}[\$rd + \text{off}] = \rs	'off' is sign extended
Jump*	00 [off (6 bits)]*	$\$PC = \$PC + \text{off}$	'off' is sign extended
NOP	11 00 XX XX	Do nothing	
Addi (Add immediate)	11 11 [rd] [imm]	$\\$rd = \\$rd + \text{imm}$	'imm' is sign extended 'imm' is 2s complement

Grading Policy

- Report (30%)
 - Explain the overall design and structure in detail
 - Specify the functionality of each module in your implementation
 - Verify your implementation is correct with simulation result
 - Around 5 pages recommended
- Completeness (70%)
 - Six instruction sequences will be used for grading. Three of them are in tb.v and the other three will be more advanced ones.
(test 0/1/2: 7 points, test 3/4: 14 points, test 5: 21 points)
- Extra credits (10%)
 - Refer to the previous slide

Term project accounts for 50% of the total lab score!

Submission Guide

- What to submit
 - CPU source code (student_id.v (Example: 2019-12345.v))
 - You may use multiple files during implementation, but please merge them into a single v file when you submit it.
 - tb.v is only for self-testing. You do not have to submit.
 - Report (student_id.pdf (Example: 2019-12345.pdf))
- Due: Before 2019. 06. 11 (Tue) 23:59
 - No delay. Late submission is not allowed.
- Please submit source code and report separately. **Do not compress.**